
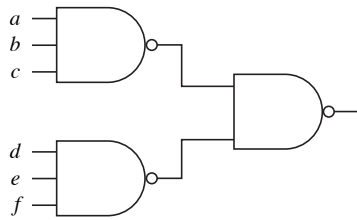


(a) An AND-OR circuit.

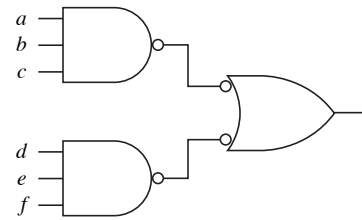

(b) The equivalent NAND-NAND circuit.



(c) The same NAND-NAND circuit as in part (b).