
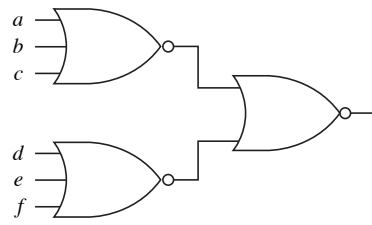


(a) An OR-AND circuit.

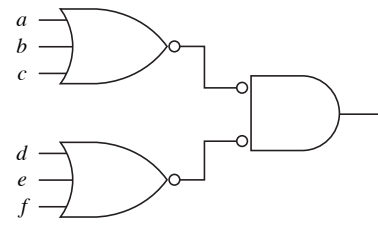

(b) The equivalent
NOR-NOR circuit.



(c) The same NOR-NOR
circuit as in part (b).

Figure 10.24