



Enable

(a) Logic diagram of enable gate.

Enable = 1	
<i>a</i>	<i>x</i>
0	0
1	1

(b) Truth table with the device turned on.

Enable = 0	
<i>a</i>	<i>x</i>
0	0
1	0

(c) Truth table with the device turned off.